

Experiment #3– Function Generator

Ava Mirmohammadmahdi 810199501
Nesa Abbasi 810199457

1.Digital to Analog conversion using PWM

1.1

```
module DAC(output reg out,input[7:0]in,input clk,rst);
    reg[7:0] counter;
    always @(posedge clk, negedge rst) begin
        if(~rst)
            counter <= 8'd0;
        else
            counter <= counter + 1'b1;
    end
    always@(counter,in)begin
        if(counter > in)
            out = 1'b0;
        else
            out = 1'b1;
    end
endmodule
```

Fig. 1 Dac verilog

1.2



Fig. 2 Dac waveform

 


Fig. 3 Dac waveform

2.Waveform Generator

 


Fig. 4 Waveform generator

 


Fig. 5 Waveform generator

1.

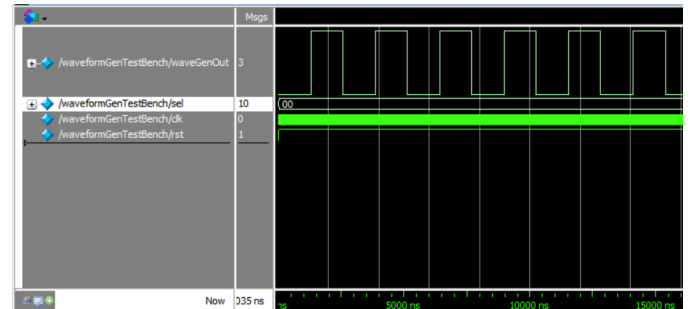


Fig. 6 Square output

 


Fig. 7 Triangle output

 


Fig. 8 Reciprocal output

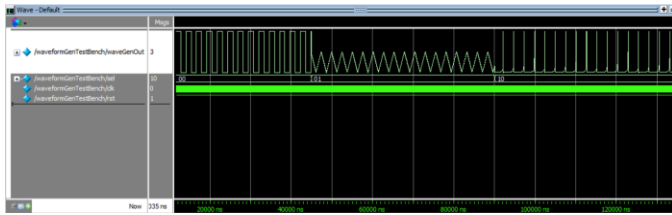


Fig. 9 Waveform generator output

2

Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat May 28 14:33:51 2022
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	WaveformGen
Top-level Entity Name	WaveformGen
Family	Cyclone IV E
Device	EP4CE6E22A7
Timing Models	Final
Total logic elements	107 / 6,272 (2 %)
Total registers	8
Total pins	12 / 92 (13 %)
Total virtual pins	0
Total memory bits	0 / 276,480 (0 %)
Embedded Multiplier 9-bit elements	0 / 30 (0 %)
Total PLLs	0 / 2 (0 %)

Fig. 10 Synthesis summary

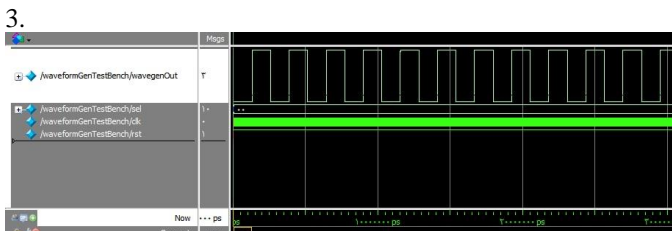


Fig. 11 Square waveform

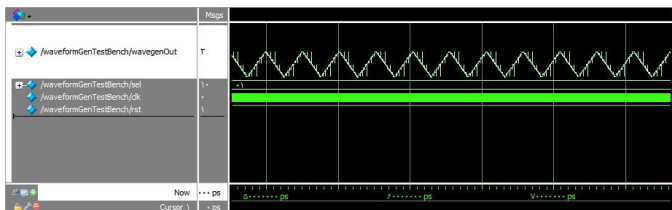


Fig. 12 Triangle waveform

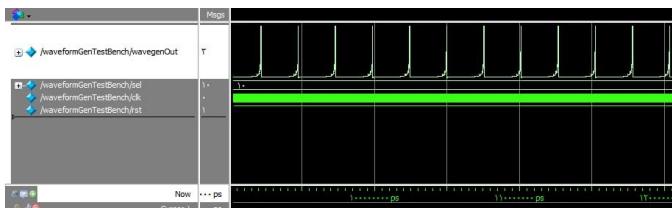


Fig. 13 Reciprocal waveform

 


Fig. 14 Sin waveform

3.Frequency Selector

 


Fig. 15 Frequency Selector

 


Fig. 16 input = 9

The 8bit Counter loads 256 – input when Co(wired to load) becomes 1. 2 least significant bits of input are 2'b00 so input = {in, 2'b00}.

Output = $256 - \{9, 2'b00\} = 256 - 9 * 4 = 220$.

 


Fig. 17 input = 56

Output = $256 - \{56, 2'b00\} = 256 - 56 * 4 = 32$.

5.

 


Fig. 18 DDS

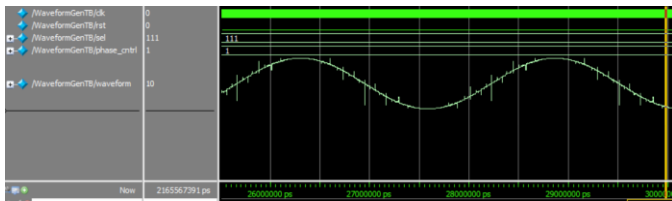


Fig. 19 Phase_ctrl = 1

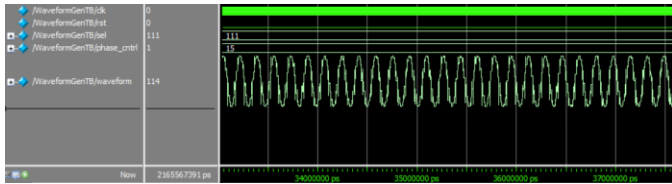


Fig. 19 Phase_ctrl = 15

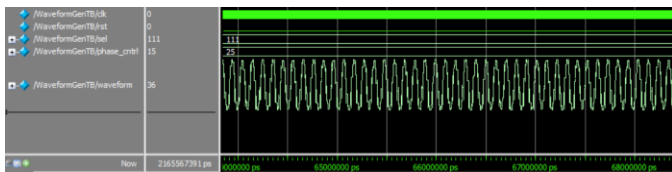


Fig. 20 Phase_ctrl = 25

When the value of Phase_ctrl is 1, every block of the rom will be shown but when the value of Phase_ctrl increases, some of the rom blocks will be skipped.

4. Amplitude Selector

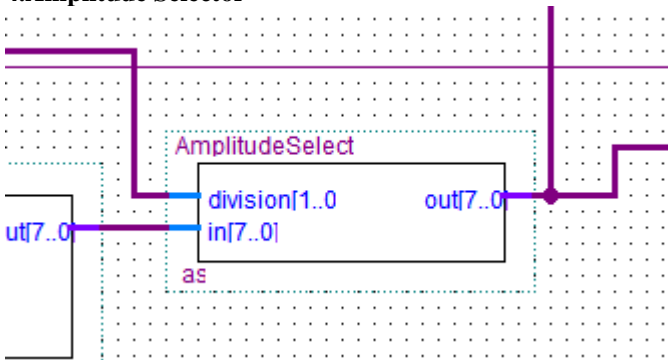


Fig. 21 amplitude selector

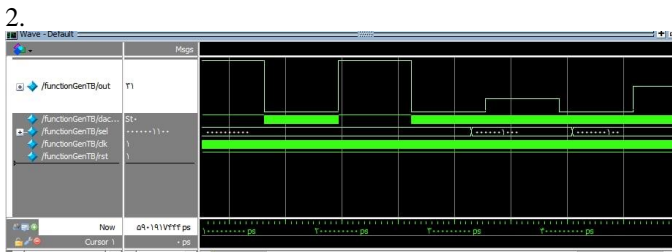


Fig. 22 Shifted Square

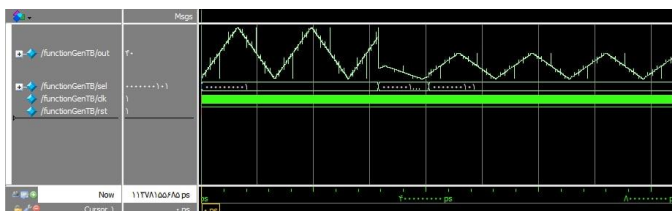


Fig. 23 Shifted Triangle

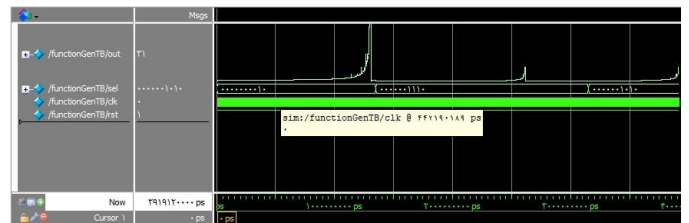


Fig. 24 Shifted Reciprocal

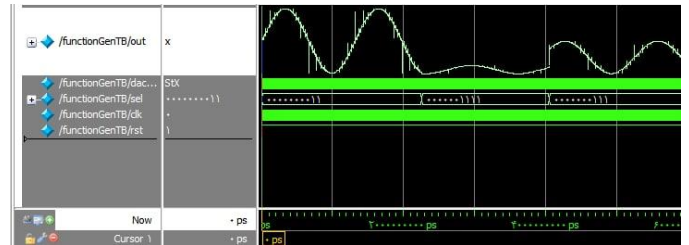


Fig. 25 Shifted Sin

5. The total design

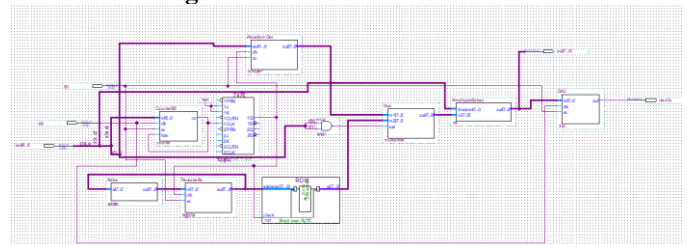


Fig. 26 Total design

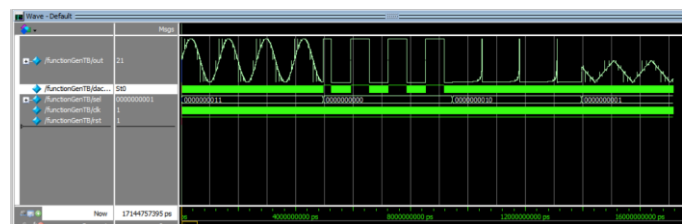


Fig. 27 Waveforms

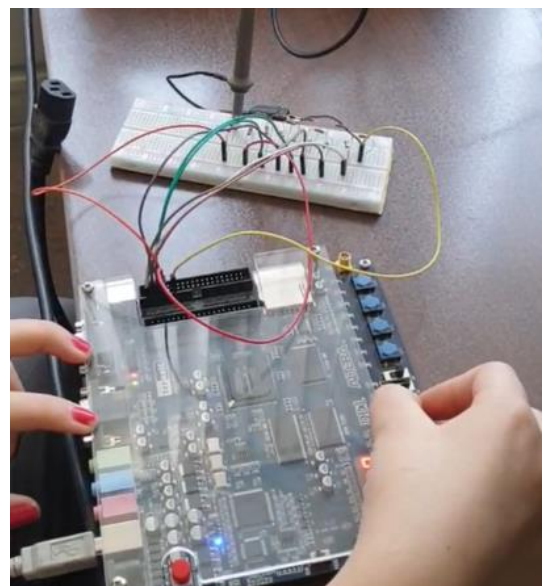


Fig. 28 Circuit

 


Fig. 29 Square Waveform without shift

 


Fig. 33 Triangle Waveform with one shift

 


Fig. 30 Square Waveform with one shift

 


Fig. 34 Triangle Waveform with two shifts

 


Fig. 31 Square Waveform with two shifts

 


Fig. 35 Reciprocal Waveform without shift

 


Fig. 32 Triangle Waveform without shift



Fig. 36 Reciprocal Waveform with one shift

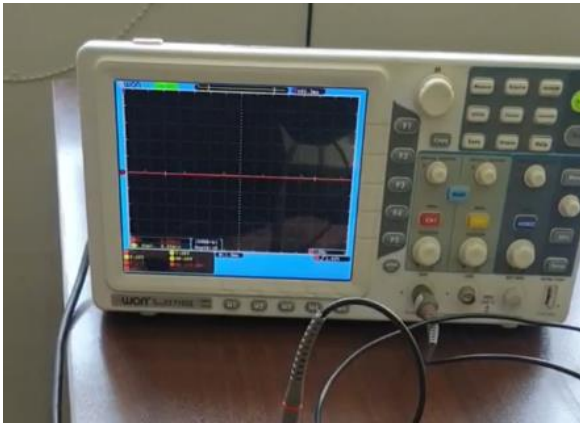


Fig. 37 Reciprocal Waveform with two shifts

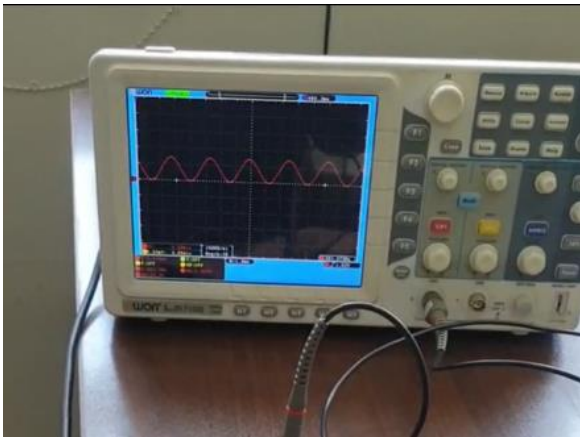


Fig. 38 Sin Waveform without shift

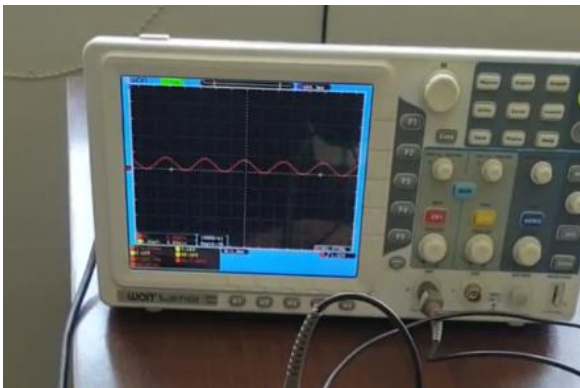


Fig. 39 Sin Waveform with one shift



Fig. 40 Sin Waveform with two shifts